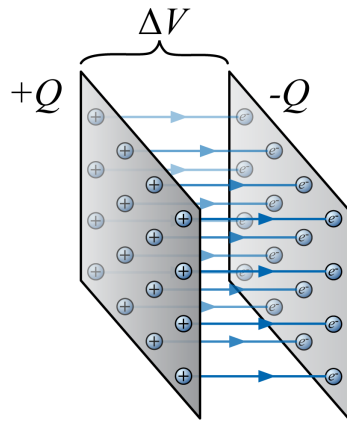



Capacitors



Capacitance

$$C := \frac{Q}{\Delta V}$$

$$[C] = \frac{C}{V} = F$$

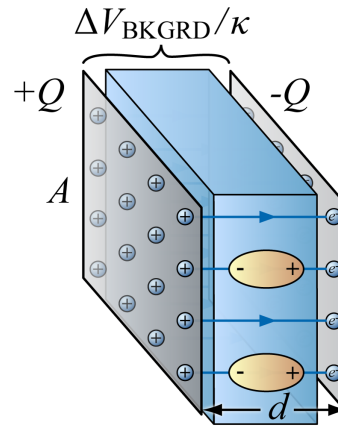


Parallel-plate capacitor

$$C_{\parallel \text{ PLATES}} = \kappa \epsilon_0 \frac{A}{d}$$

$$|\vec{E}_{\parallel, \text{BKGRD}}| = \frac{Q}{\epsilon_0 A}$$

$$|\vec{E}| = \frac{|\vec{E}_{\text{BKGRD}}|}{\kappa}$$

Storing energy in a capacitor

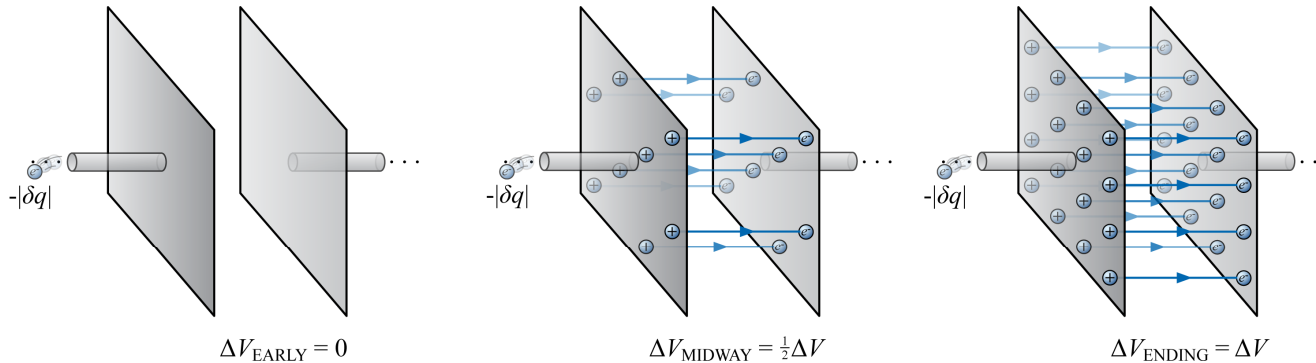

$$\Delta W_{\text{HAND}} = |\delta q|0 + \dots + |\delta q| \left| \frac{1}{2} \Delta V \right| + \dots + |\delta q| |\Delta V|$$


$$= Q \left[\frac{|\delta q|}{Q} 0 + \dots + \frac{|\delta q|}{Q} \left| \frac{1}{2} \Delta V \right| + \dots + \frac{|\delta q|}{Q} |\Delta V| \right]$$

$$\Delta U_C = Q \left(\frac{1}{2} \Delta V \right) = \frac{1}{2} C (\Delta V)^2 = \frac{Q^2}{2C}$$


Capacitors

Capacitors in circuits

Single capacitor

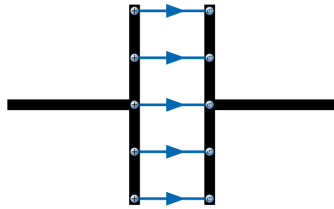

Capacitors in parallel

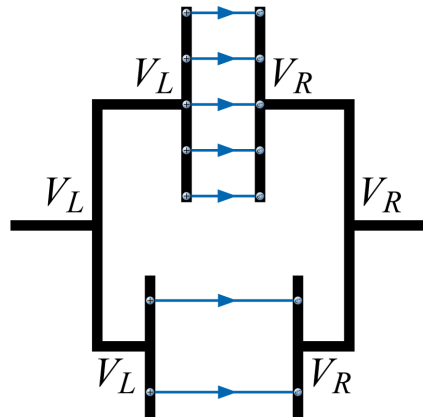


Each capacitor has same ΔV


$$C_{EQ,||} = C_1 + C_2 + \dots$$

Q_{EQ} divides so that $Q_i \propto C_i$

Capacitors in series

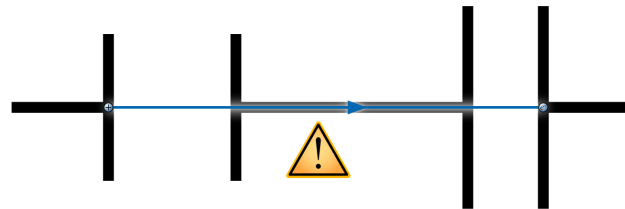

$|\vec{E}|$ should quickly approach 0 in conductor
(quickly achieves electrostatic equilibrium)

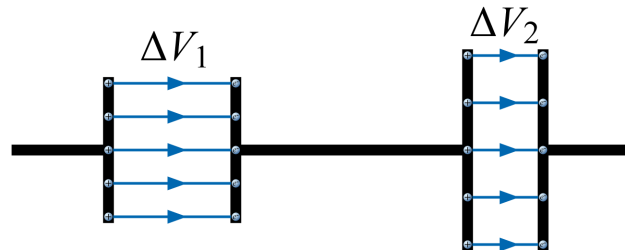

Each capacitor has same Q

$$\frac{1}{C_{EQ,SER}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots$$

ΔV_{EQ} divides so that $\Delta V_i \propto \frac{1}{C_i}$