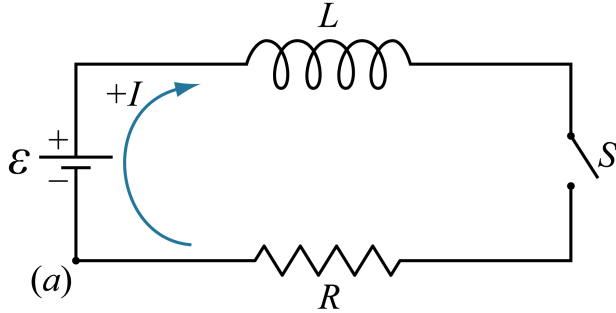


Increasing current over time in an LR series circuit



$$\Delta V_{\text{LOOP}} = 0$$

$$+\varepsilon - L \frac{dI}{dt} - IR = 0$$

| Early times (just after closing "S") | Intermediate time t | Late times (long after closing "S") | | | | | | | | | |
|---|---|---|------|---------|---------|-----------|-----------|-------|-----------|-----------|---|
| $+\varepsilon - L \frac{dI}{dt} - \underbrace{I}_0 R = 0$ | $+\varepsilon - L \frac{dI}{dt} - IR = 0$ | $+\varepsilon - L \frac{dI}{dt} - IR = 0$ | | | | | | | | | |
| <p>Inductor: $I_0 = 0, \Delta V_0 = \varepsilon$</p> <p>Resistor: $I_0 = 0, \Delta V_0 = 0$</p> | $-L \frac{dI}{dt} = IR - \varepsilon$ $-\left(\frac{L}{R}\right) \frac{dI}{dt} = I - \left(\frac{\varepsilon}{R}\right)$ $-\tau \int_{I=I_i}^{I=I_f} \frac{1}{I - I_\infty} dI = \int_{t=t_i}^{t=t_f} dt$ $-\tau [\ln I - I_\infty]_{I=I_i}^{I=I_f} = t_f - t_i$ <p>Note: $I - I_\infty < 0$</p> $-\tau \ln\left(\frac{I_\infty - I_f}{I_\infty - I_i}\right) = t_f - t_i$ <table border="1" data-bbox="639 1234 967 1373"> <thead> <tr> <th></th> <th>Time</th> <th>Current</th> </tr> </thead> <tbody> <tr> <td>Initial</td> <td>$t_i = 0$</td> <td>$I_i = 0$</td> </tr> <tr> <td>Final</td> <td>$t_f = t$</td> <td>$I_f = I$</td> </tr> </tbody> </table> $I = \left(\frac{\varepsilon}{R}\right) \left[1 - e^{-\frac{t}{\tau}}\right]$ | | Time | Current | Initial | $t_i = 0$ | $I_i = 0$ | Final | $t_f = t$ | $I_f = I$ | <p>Inductor: $I_\infty = \frac{\varepsilon}{R}, \Delta V_\infty = 0$</p> <p>Resistor: $I_\infty = \frac{\varepsilon}{R}, \Delta V_\infty = \varepsilon$</p> |
| | Time | Current | | | | | | | | | |
| Initial | $t_i = 0$ | $I_i = 0$ | | | | | | | | | |
| Final | $t_f = t$ | $I_f = I$ | | | | | | | | | |

